

Golden Arduino

Objective:

A board like Arduino Uno was designed with a focus on modular separation and enhanced debugging capabilities, featuring additional test points to simplify the debugging process during development and testing phases. Industry best practices were implemented, including the integration of a separate ground plane, essential decoupling, and low-pass filter capacitors, and minimizing cross-under. Routing for Tx and Rx traces was optimized by treating them as differential pairs, thereby improving signal integrity, and reducing electromagnetic interference such as cross talk. Strategic component placement was employed during board bring-up to enhance performance, mitigate ground bounce, and minimize electromagnetic noise.

Plan of record:

- 5V power input rating from either power jack or USB-mini.
- LDO to regulate voltage to 3.3V.
- Sense resistor to measure inrush current.
- 12MHz oscillator for USB data transmission.
- 16MHz oscillator for system clock.
- USB to UART communications to upload sketches.
- Circuit for microcontroller reset.
- Ferrite beads to reduce noise on AVCC.
- Bypass capacitors to compensate for the current surge in power rail.
- Low pass filters.
- LED indicators
- Circuit to avoid switch debouncing.
- Jump start circuit for oscillators.

Risk reduction:

- Added LEDs to indicate power supply is working fine.
- ESD protection to USB mini port.
- Proper labelling for each input and outputs.
- Added test points to each module to read measurements and verify the functionality of module.

What does it mean to work:


- Obtaining a 5V power supply from the power jack and USB mini.
- Measuring the 3.3V output from the LDO regulator.
- Utilizing a 12MHz frequency oscillator for the USB data transmission.
- Utilizing a 16MHz oscillator frequency for the system clock.
- Data transmission via D+ and D- pins.
- Data transmission via Tx and Rx.
- Implementing proper microcontroller reset without debouncing.
- Ensuring that LED indicators are working fine.
- Achieving reduced ground bounce compared to a commercial board.
- Achieving reduced power rail noise compared to a commercial board.

PCB REPORT – BOARD 3

Component listing:

- Microcontroller: Atmega328p
- USB to TTL converter: CH340g
- Crystal oscillator: 12MHz, 16MHz
- Capacitor: 22pF, 1uF, 10uF, 22uF
- Resistor: 500m, 1K, 10K, 1M
- Inductor: 10uH
- Headers
- LEDs: Red
- Switch: push button
- Power jack and USB mini



Schematic:

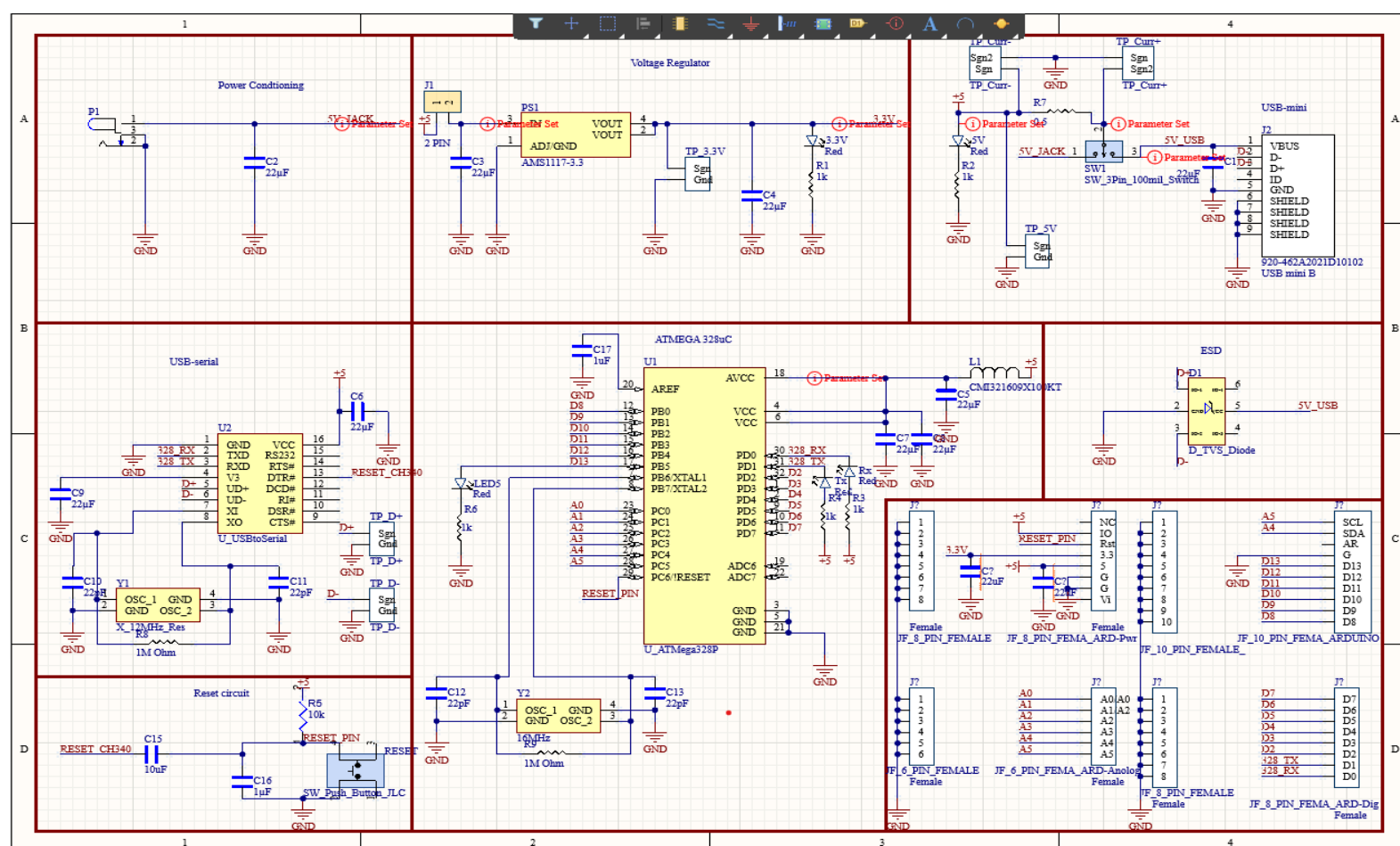

Circuit involved in Golden Arduino board.

PCB REPORT – BOARD 3

Layout:

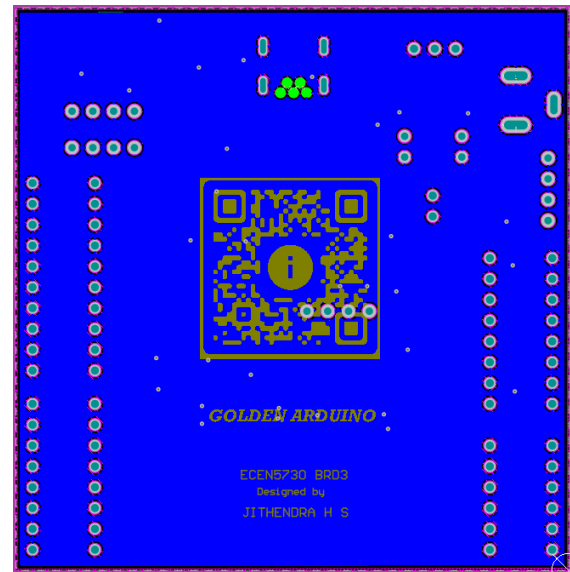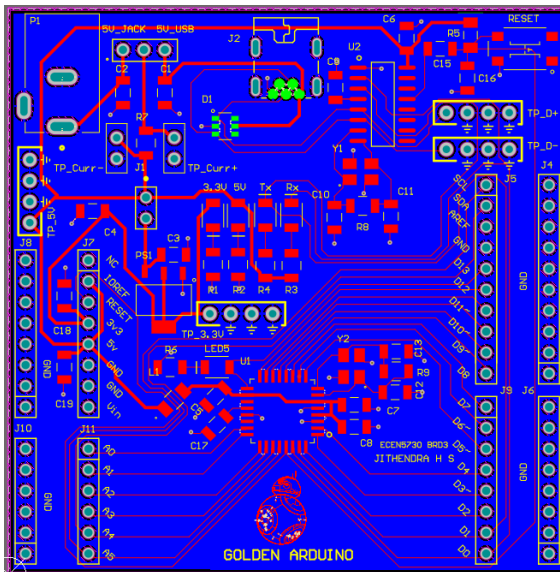

Board:

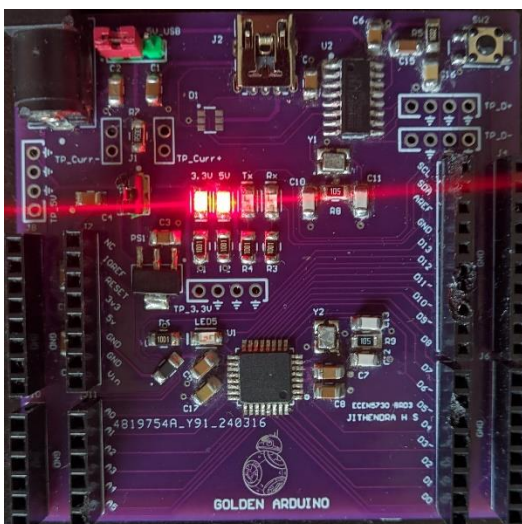
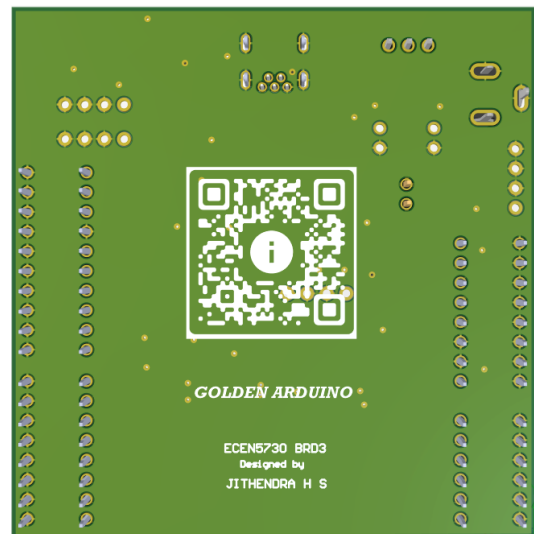
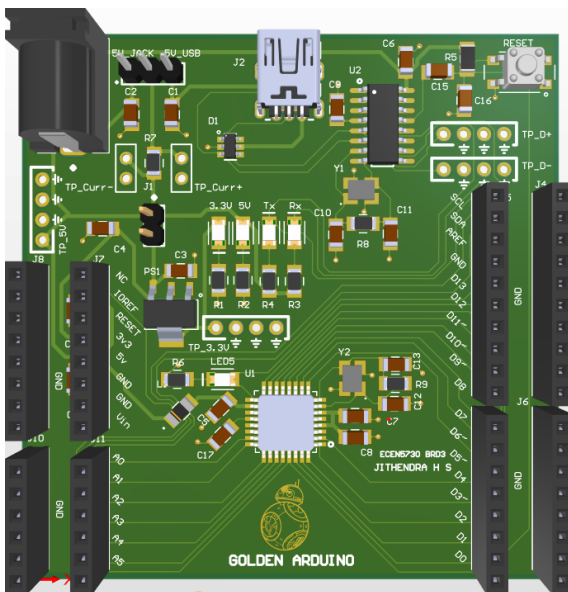
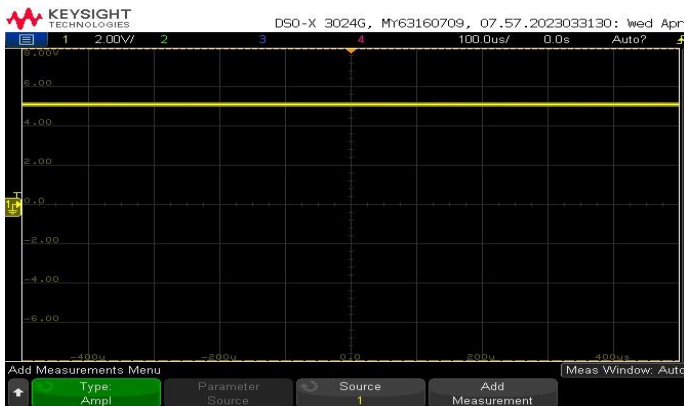
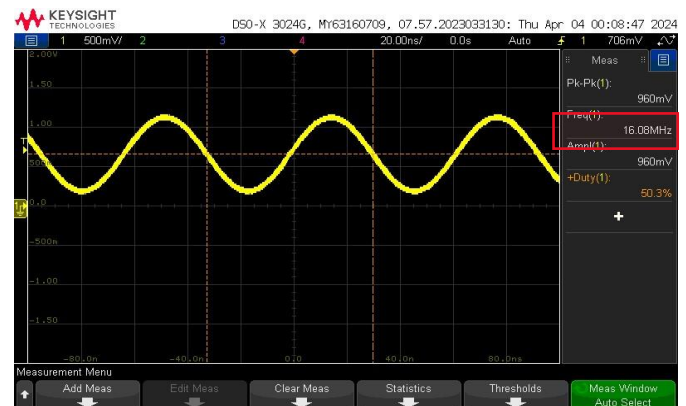
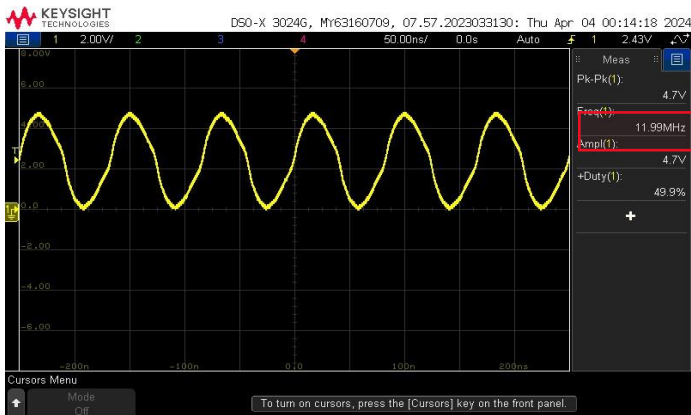



Figure 1.1 Assembled board with LEDs lit up.

Scope output:**1. 5V and 3.3V power supply:**

Measured and verified that 5V DC voltage is coming from the power jack and USB mini, which is then converted to 3.3V by the LDO.

2. Oscillators:

Observed a clock signal of frequency 12MHz generated by the oscillator used for USB data transmission and 16MHz generated by the oscillator used for the system clock.

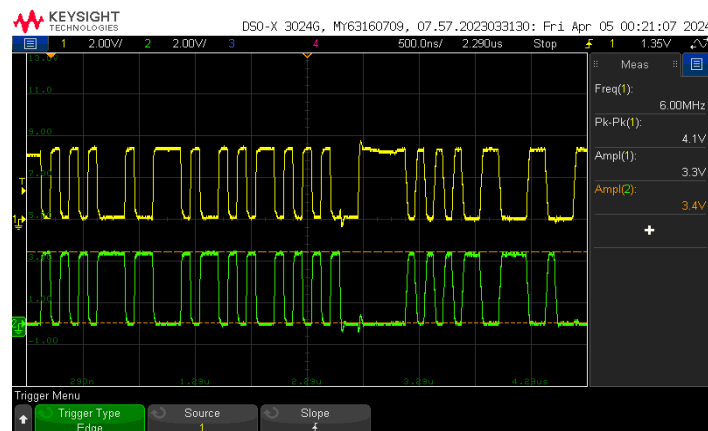3. USB mini output:

Seen keepalive signal received from D+ and D- of the USB port every 1ms.

The figure displays two windows from a computer screen. The top window is a Keysight Oscilloscope showing a square wave signal on a black background. The signal is yellow and has a period of approximately 1.9231 kHz. The vertical scale is 5.0V, and the horizontal scale is 200.0ns. The signal is labeled 'Low signal' in red. The bottom window is an Arduino IDE showing a C++ program that reads an analog input on pin 0 and prints the result to the Serial Monitor. The Serial Monitor shows a stream of data points, such as '10:56:34.699 -> 88', indicating the sensor's output over time.

Keysight Oscilloscope Data:

Measurement	Value
Freq(1)	1.9231kHz
Pk-Pk(1)	5.7V
Ampl(1)	5.0V
Ampl(2)	Low signal

Arduino IDE Code:

```

AnalogReadSerial
/*
  Reads an analog input on pin 0, prints the result to the Serial Monitor.
  Graphical representation is available using Serial Plotter (Tools > Serial Plotter menu).
  Attach the center pin of a potentiometer to pin A0, and the outside pins to +5V and ground.

  This example code is in the public domain.

  https://www.arduino.cc/en/Tutorial/multiTextExamples/AnalogReadSerial
  */

// the setup routine runs once when you press reset:
void setup() {
  // Initialize serial communication at 9600 bits per second:
  Serial.begin(9600);
}



// the loop routine runs over and over again forever:
void loop() {
  // read the input on analog pin 0:
  int sensorValue = analogRead(A0);
  // print out the value you read:
  Serial.println(sensorValue);
  delay(1);        // delay in between reads for stability
}
  
```

Serial Monitor Output:

```


10:56:34.699 -> 88
10:56:34.699 -> 86
10:56:34.699 -> 88
10:56:34.699 -> 90
10:56:34.699 -> 88
10:56:34.699 -> 86
10:56:34.699 -> 88
10:56:34.699 -> 90
10:56:34.699 -> 88
10:56:34.699 -> 86
10:56:34.699 -> 90
10:56:34.699 -> 88
10:56:34.699 -> 86
10:56:34.699 -> 90
10:56:34.745 -> 88
10:56:34.745 -> 86
10:56:34.745 -> 88
10:56:34.745 -> 90
10:56:34.745 -> 88
10:56:34.745 -> 86
10:56:34.745 -> 88
10:56:34.745 -> 90
  
```

5. Steady and In-rush current

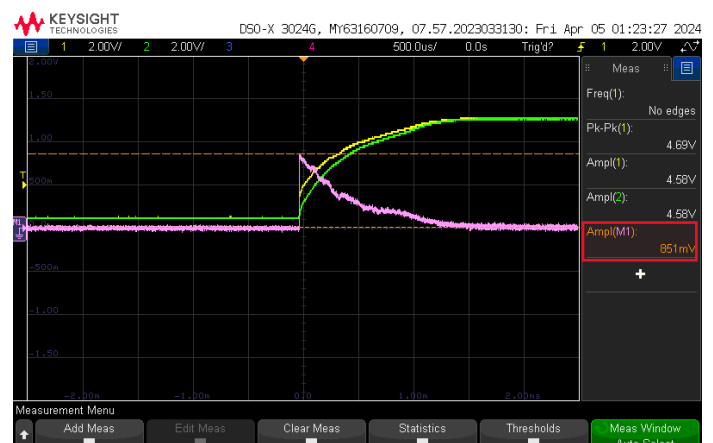
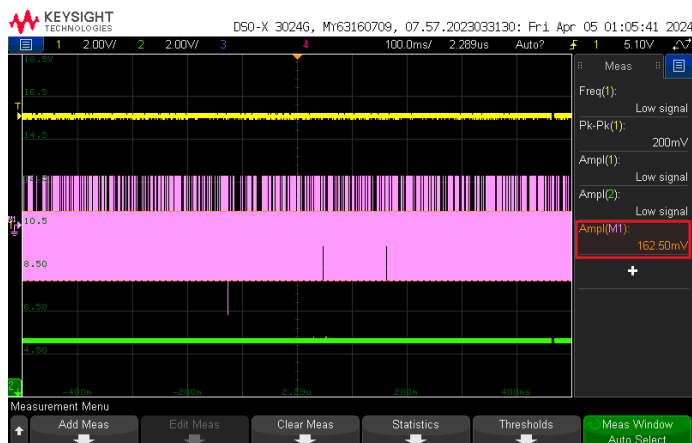


With the help of the noise shield provided below, we evaluated the performance of the Golden Arduino compared to a Commercial Arduino.



PCB REPORT – BOARD 3

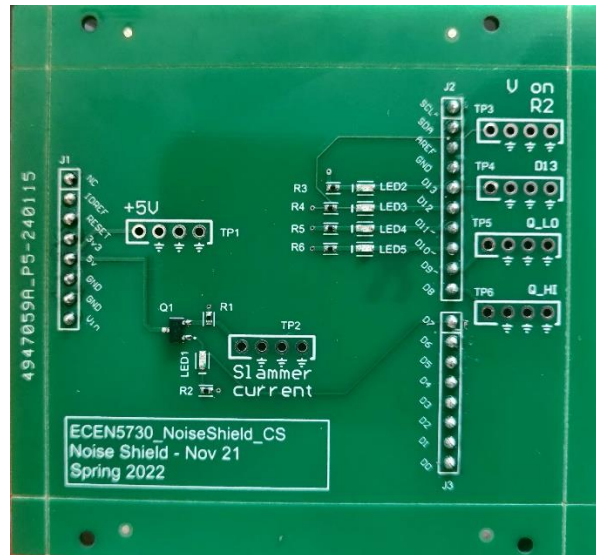

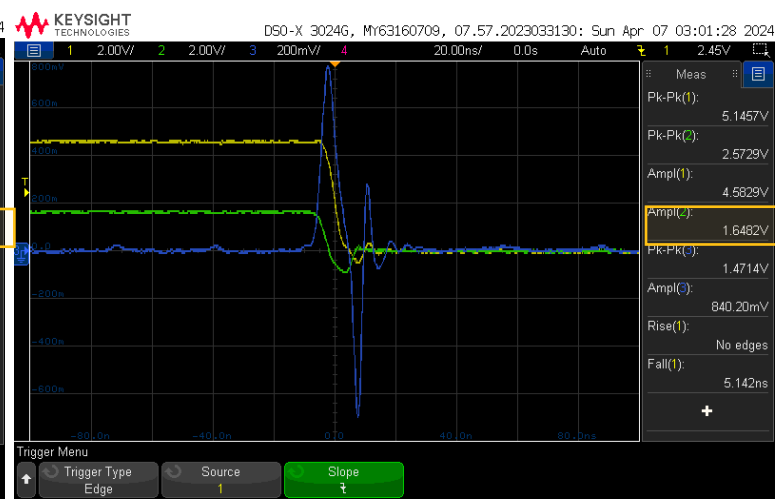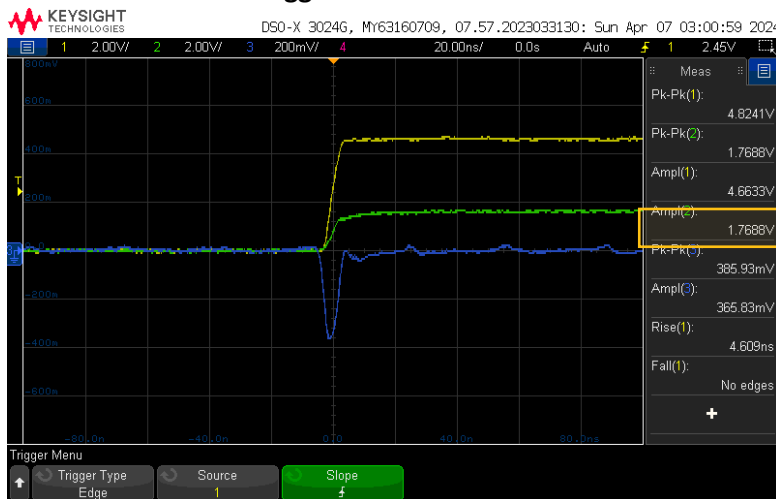6. Quiet Low output observed with a greater number of switching digital pins acting as aggressors:



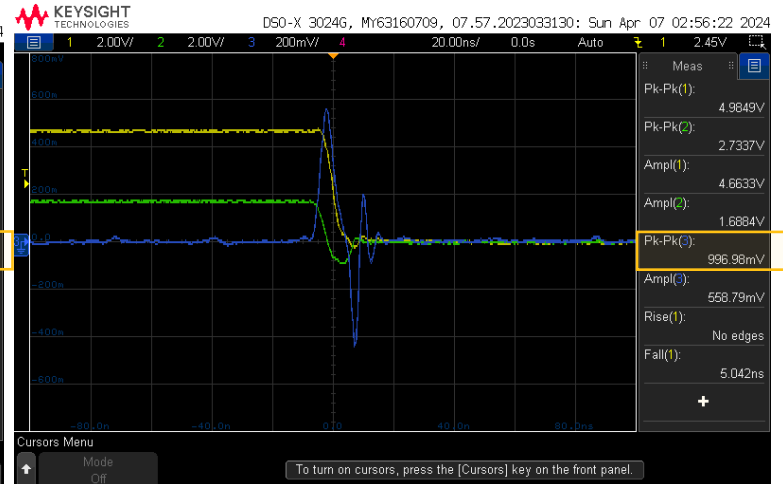
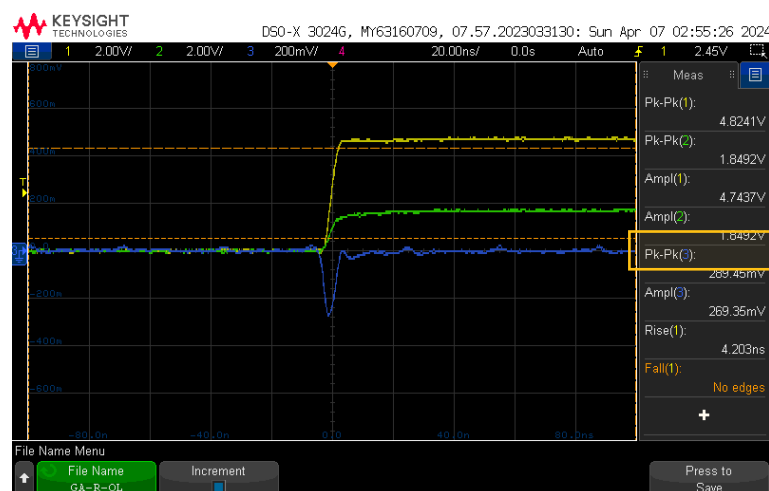
From the commercial board, observed ground bounce noise of about **385.93mV** and **1.47V** on the quiet low digital pin.





From the Golden Arduino board, observed ground bounce noise of about **289.45mV** and **996.98mV** on the quiet low digital pin.

PCB REPORT – BOARD 3

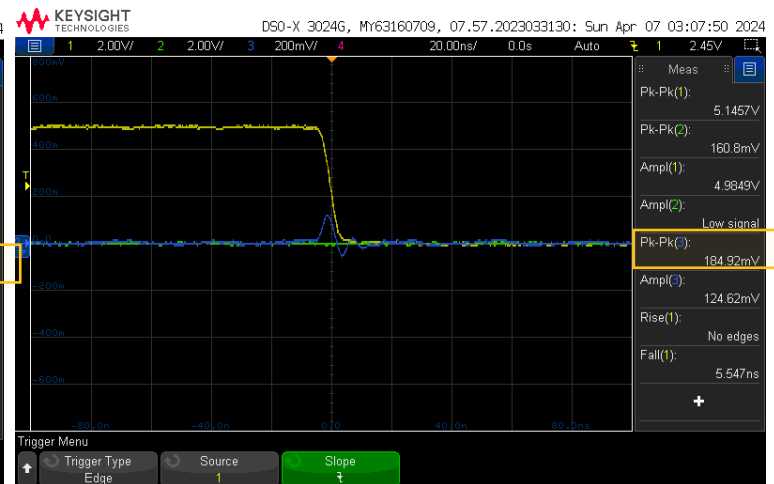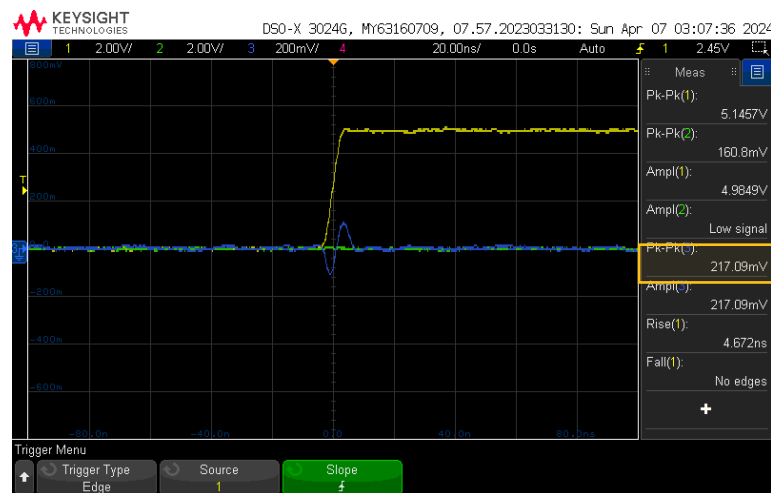7. Quiet Low output observed with just one digital pin acting as an aggressor:





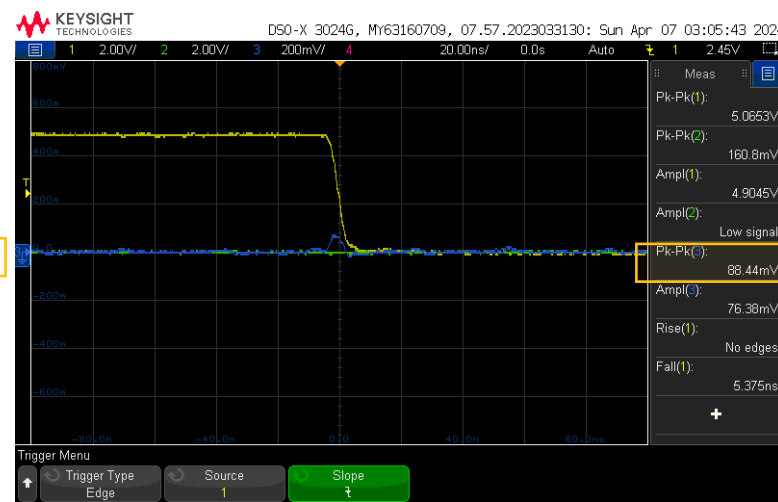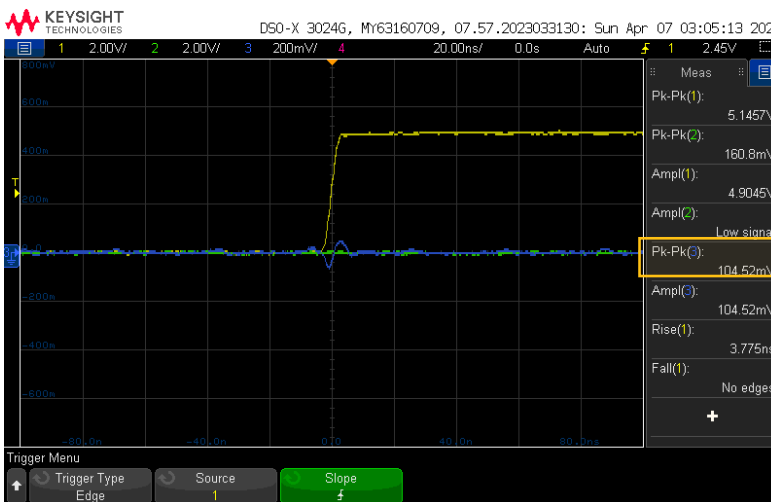From the commercial board, observed ground bounce noise of about **217mV** and **184mV** on the quiet low digital pin.




From the Golden Arduino board, observed ground bounce noise of about **104.52mV** and **88.44mV** on the quiet low digital pin.

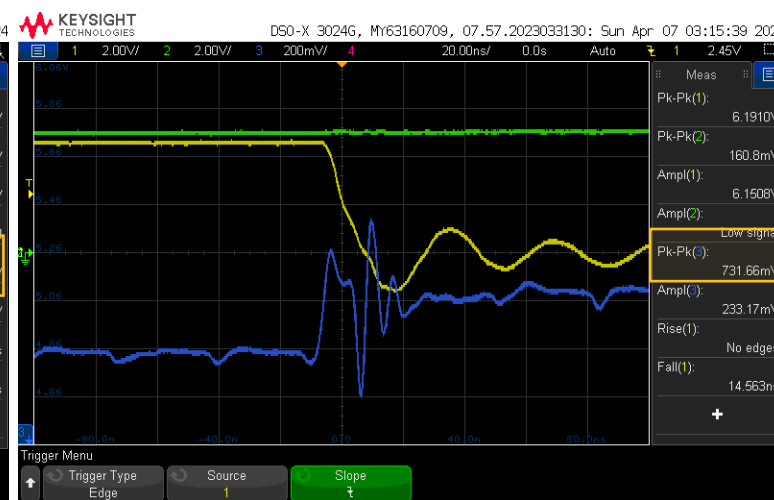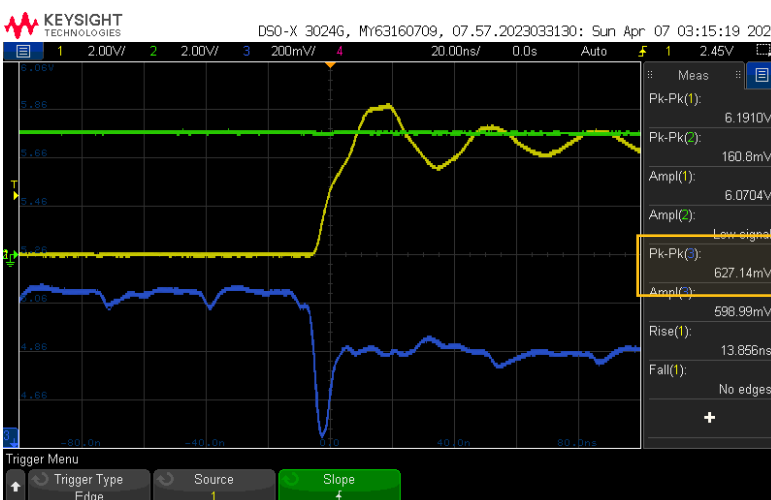8. Quiet High output observed with the IC acting as an aggressor:




PCB REPORT – BOARD 3

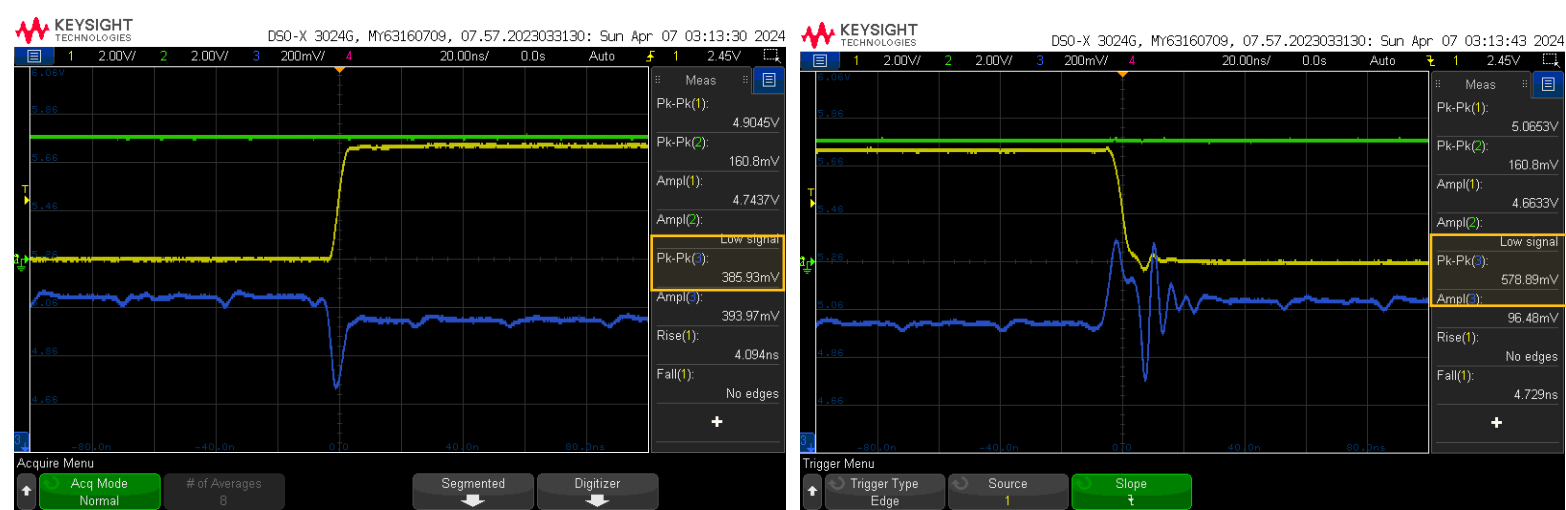From the commercial board, observed power rail noise of about **627mV** and **731.66mV** on the quiet high digital pin.




From the Golden Arduino board, observed power rail noise of about **385.93mV** and **578.89mV** on the quiet high digital pin.

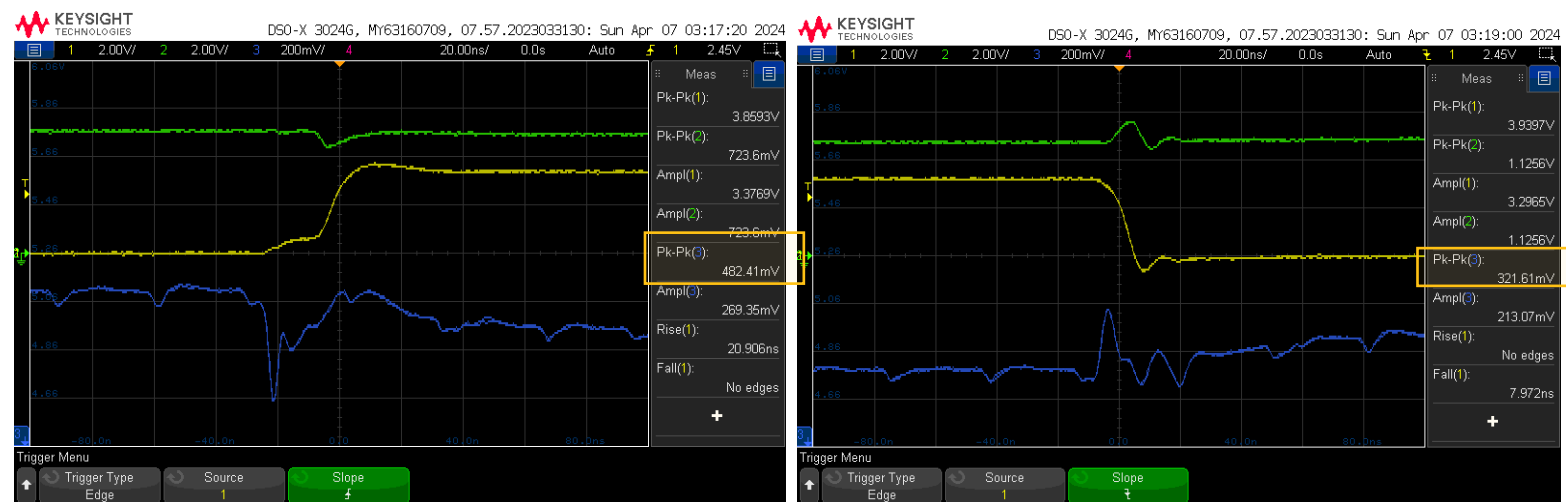9. Quiet High output observed with the entire board acting as an aggressor:




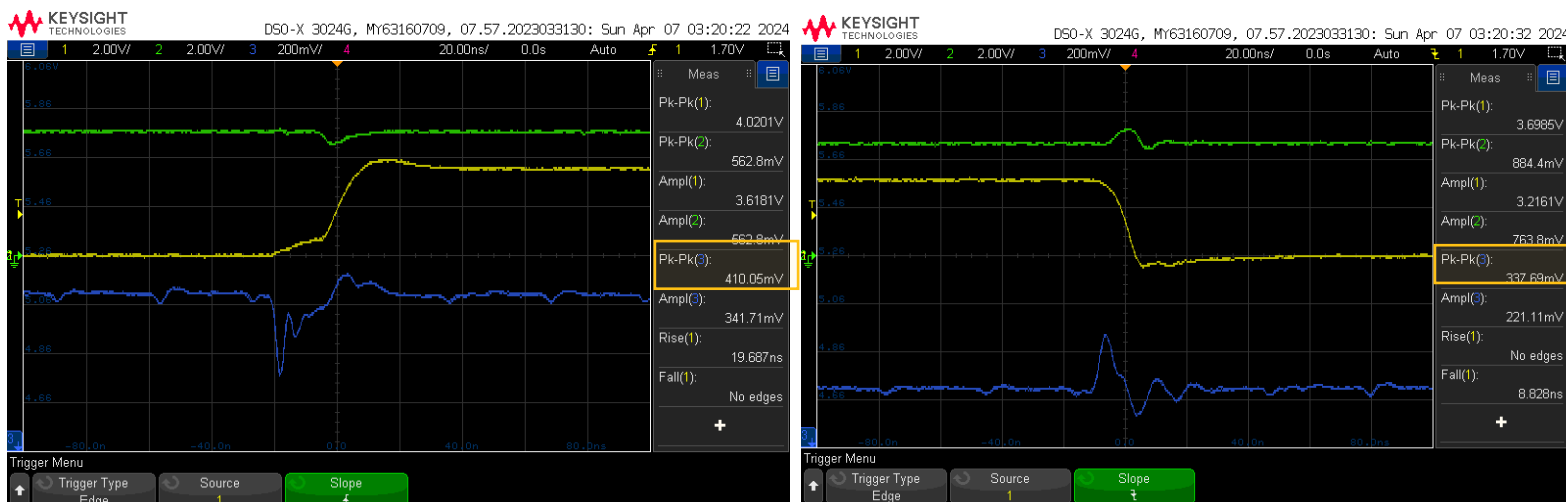
From the commercial board, observed power rail noise of about **482.41mV** and **321.6mV** on the quiet high digital pin.





PCB REPORT – BOARD 3

From the Golden Arduino board, observed power rail noise of about **410mV** and **337.69mV** on the quiet high digital pin.

10. Near field emissions:

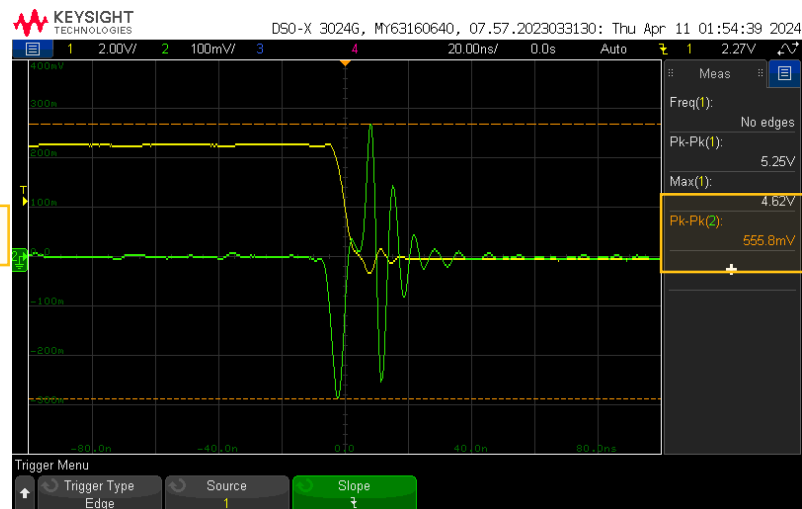
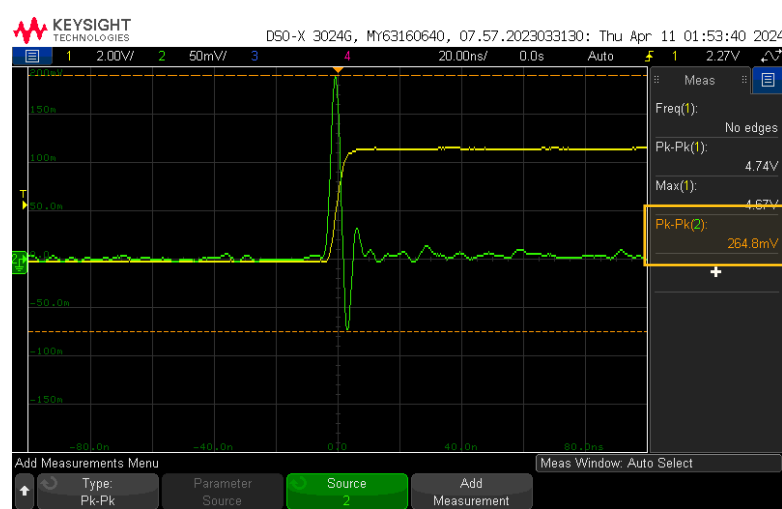


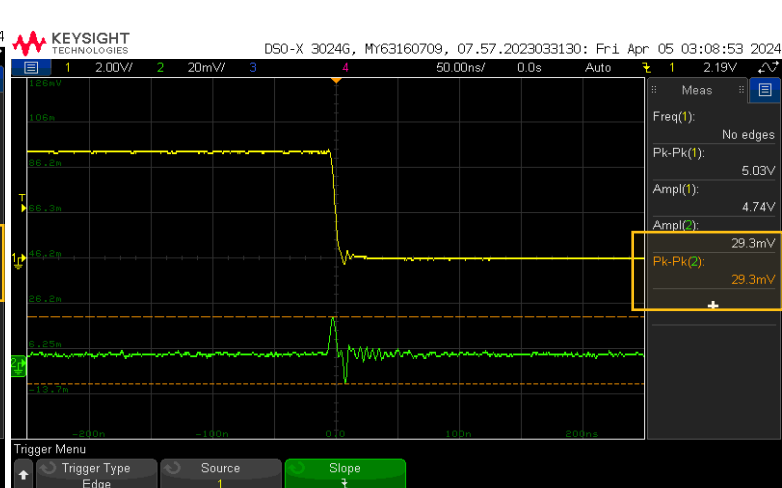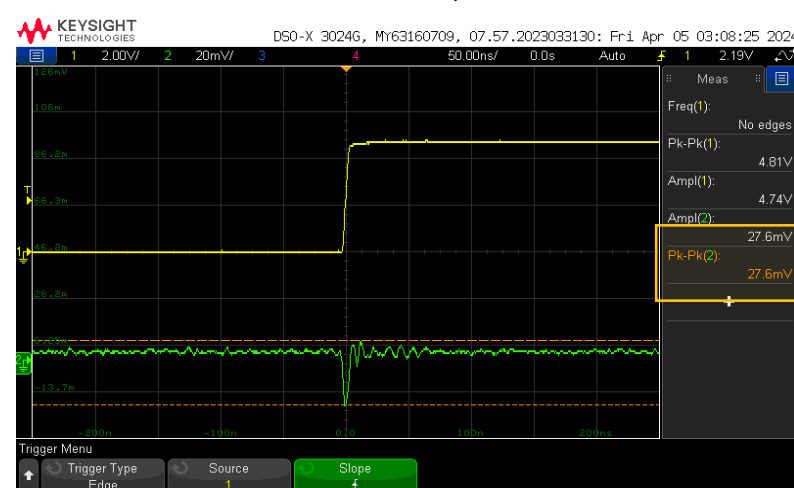From the Commercial Arduino board, observed around **264.8mV** and **555.8mV** of NFE (near field emission).




From the Golden Arduino, observed around **27.6mV** and **29.3mV** of NFE (near field emission). Moreover the maximum noise is produced from switching digital pin.

11. Digital pin output:

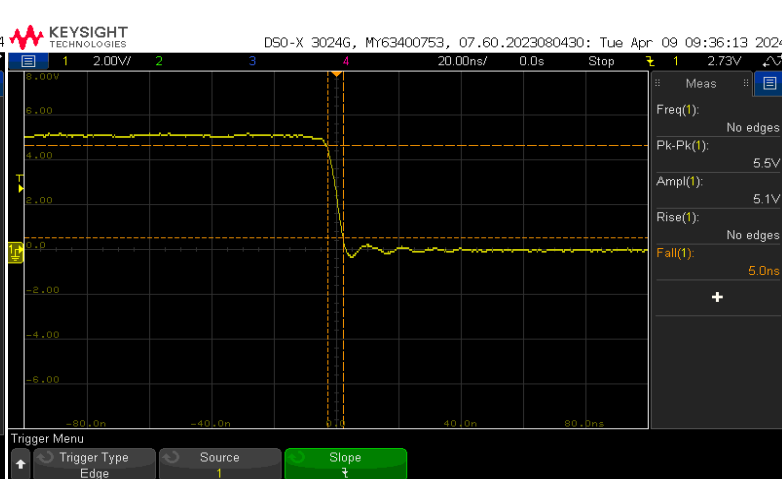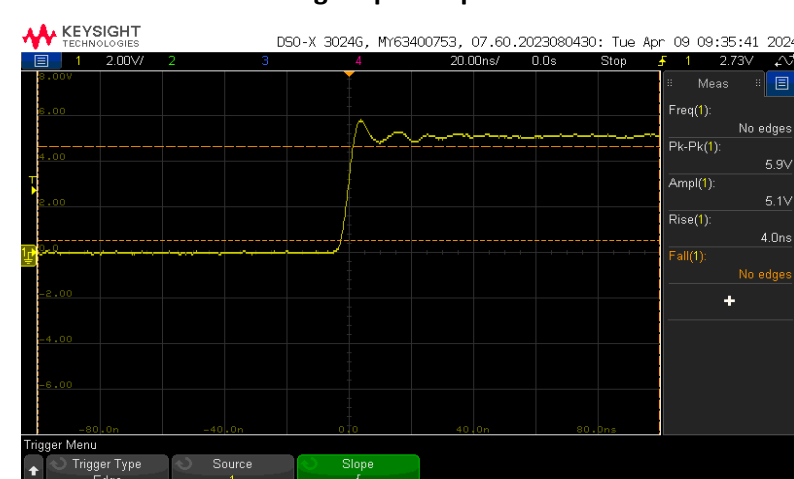


PCB REPORT – BOARD 3

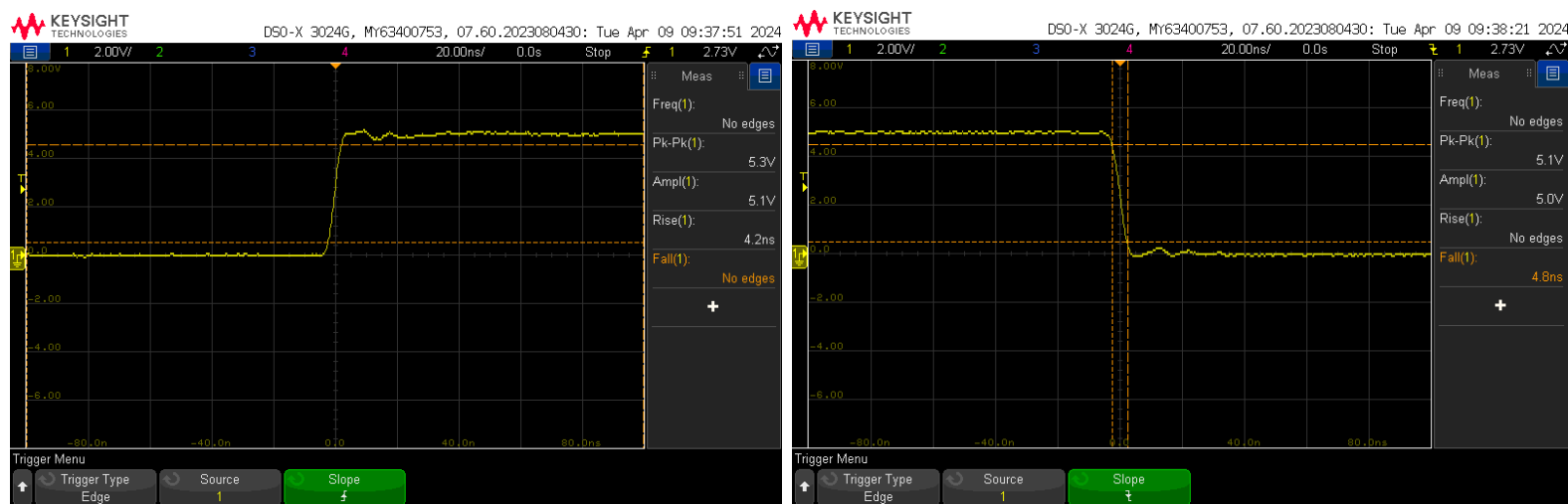In the commercial board, a rise time of 4ns and fall time of 5ns were observed when digital pin 13 was triggered to output a signal of 5Hz.




The rise time of 4.2ns and fall time of 4.8ns were noted when digital pin 13 is triggered to output a signal of 5Hz on the Golden Arduino board. This signifies that there is not much difference in signal timing characteristics between the Golden Arduino and the commercial board. Otherwise, it could lead to jitter in high-frequency communication signal transmission.

12. Reset pin:

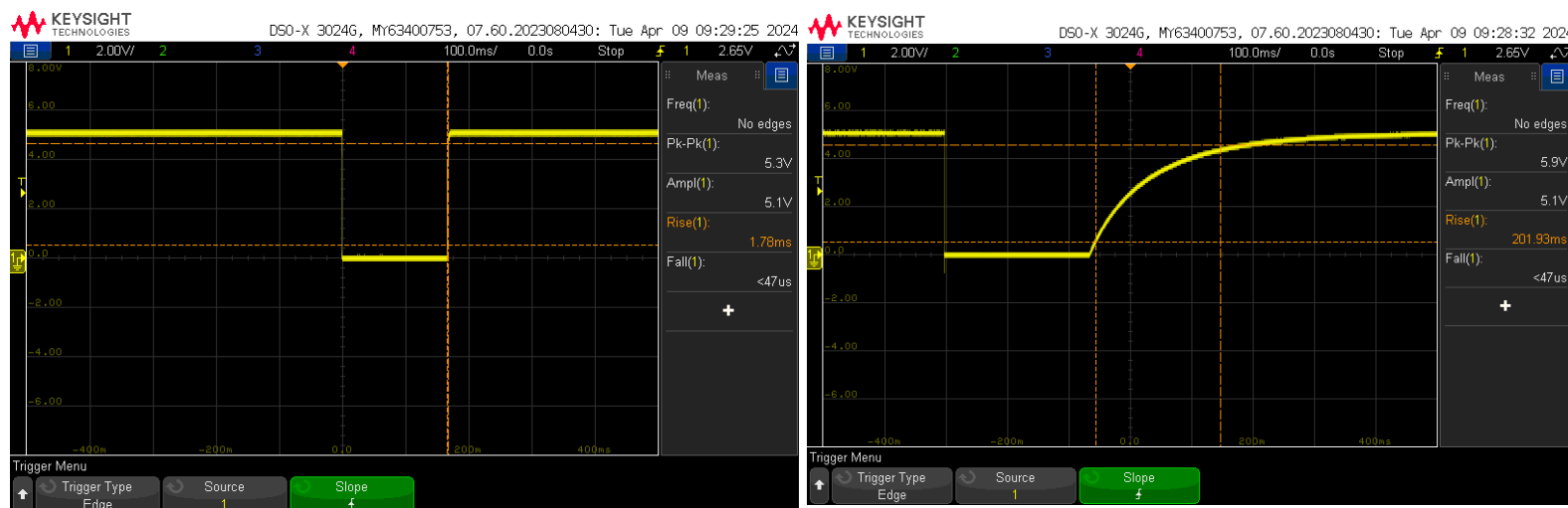

Observed a rise time of 1.78ms at the commercial board to reach logic high once the reset button is pressed. Similarly, a rise time of 201.93ms was observed at the Golden Arduino board, demonstrating better control over switch debouncing. Both boards maintain the reset pin low for more than 10 microseconds as required by the microcontroller.

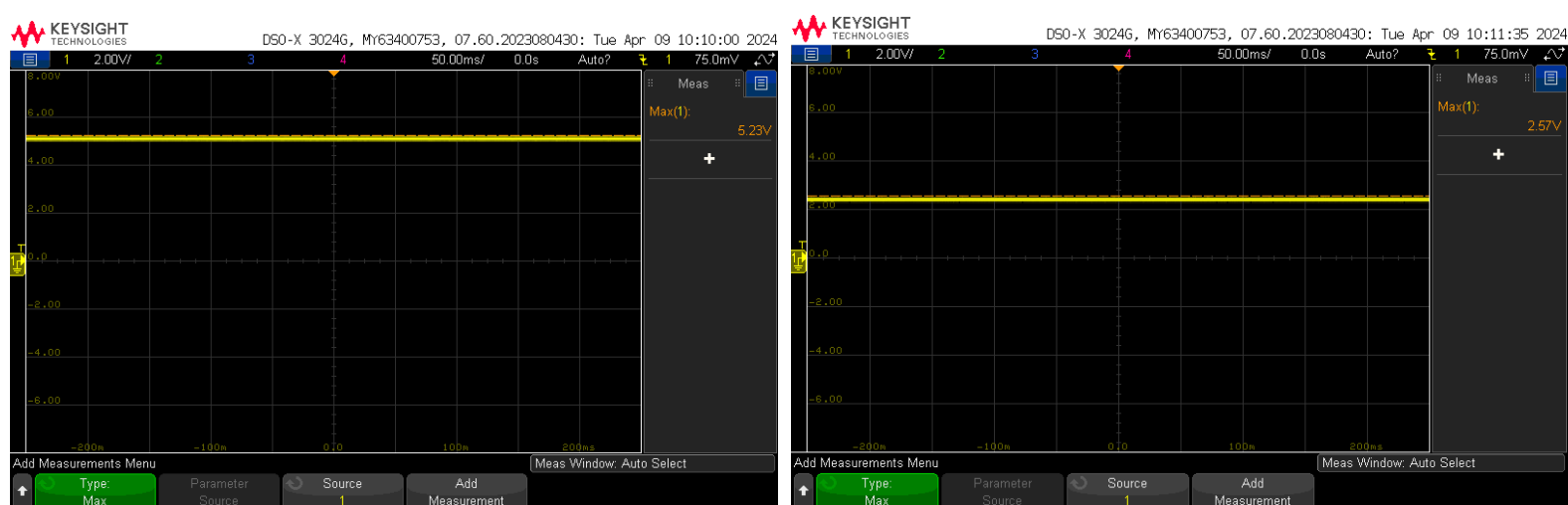13. Thevenin resistance and voltage at digital pin 12:

The Thevenin voltage measured about 5.23V. After adding a 330ohm resistor as a load, the calculated load voltage is about 2.57V. Therefore, the Thevenin resistance (internal resistance of the voltage source, here microcontroller) is **34.15 ohms**.

14. Noise summary of Commercial Board and Golden Arduino:

Parameter	Trigger edge	Commercial board	Golden Arduino	Change in noise (%)
Current through 50ohm resistor	rise	37mA	35mA	
	fall	34mA	35mA	
Quiet Low with multiple aggressors	rise	386mV	290mV	25
	fall	1.47V	997mV	32
Quiet Low with single aggressors	rise	217mV	185mV	14
	fall	105mV	88 mV	15
Quiet High with micro controller as aggressor	rise	627mV	386mV	38
	fall	732mV	579mV	20
Quiet High with whole board as aggressor	rise	482mV	410mV	15
	fall	322mV	338mV	4
Near Field emission	rise	265mV	28mV	89.5
	fall	556mV	29mV	95

15. What All worked

characteristics	Result	Remarks
Obtaining a 5V power supply from the power jack and USB mini.	Worked	
Measuring the 3.3V output from the LDO regulator.	Worked	
Utilizing a 12MHz frequency oscillator for the USB data transmission.	Worked	

PCB REPORT – BOARD 3

Utilizing a 16MHz frequency oscillator for the system clock.	Worked	
Data transmission via D+ and D- pins.	Worked	
Data transmission via Tx and Rx.	Worked	
Implementing proper microcontroller reset without debouncing.	Worked	
Ensuring that LED indicators are working fine.	Worked	
Reduced ground bounce compared to commercial board.	Worked	
Achieving reduced ground bounce compared to a commercial board.	Worked	
Achieving reduced power rail noise compared to a commercial board.	Worked	

16. Mistakes

- Missed labelling the reset switch.
- Placed components too close to each other, which made soldering the components difficult.
- Forgot to add independent ICSP pins.

17. Key learnings

- Prototype Design: Practicing the entire design flow to gain hands-on experience.
- Datasheet Reading: Extracting useful information while navigating ambiguity.
- Feature Incorporation: Adding extra features to enhance functionality and evaluation options.
- Prototype Elements: Including test points, LEDs, and isolation switches for testing and debugging.
- Initial Design Phase: Beginning with POR, sourcing non-commodity parts, and prototyping on breadboards.
- Signal Routing: Employing best practices to minimize cross talk and power rail noise by avoiding cross under.
- Board Improvements: Identifying areas for enhancement in commercial boards to optimize performance.
- Inrush Current Measurement: Understanding and measuring inrush current to prevent damage to components and ensure proper functioning of the circuit.
- Importance of Differential Pairs: Recognizing the significance of using differential pairs to minimize noise and improve signal integrity in high-speed communication lines.
- Microcontroller Boot loading: Learning the process of boot loading a microcontroller to load firmware onto it, enabling it to execute specific tasks upon startup.